

# JOB SHEET

Name \_\_\_\_\_ Class \_\_\_\_\_ Div. \_\_\_\_\_ Date \_\_\_\_\_

Sub. \_\_\_\_\_ Roll No. \_\_\_\_\_ Topic \_\_\_\_\_ Page No. \_\_\_\_\_

Name: Hardik Shah Roll No: 18010221025

Batch: D2

Name of the experiment: Staircase wiring.

Tools & Requirements: Goggles, rubber gloves, screwdriver, test, pliers and screws.

Raw materials: Two way switches, bulb holders, bulb joint clips, wires, switch board.

Procedure:

- ① Mark switch and bulb location points and draw lines for wiring on the wooden board.
- ② Place wires along the lines and fix them with the help of clips.
- ③ Fix two way switches and the bulb holders and the bulb holders at the marked position on the wooden board. at the max
- ④ Similarly complete the entire wiring system using circuit diagram.
- ⑤ Test the working of bulbs by giving electric supply to the circuit.

⇒ NOTE different cases and conditions in the table:



Name \_\_\_\_\_ Class \_\_\_\_\_ Div. \_\_\_\_\_ Date \_\_\_\_\_  
Sub. \_\_\_\_\_ Roll No. \_\_\_\_\_ Topic \_\_\_\_\_ Page No. \_\_\_\_\_

SWITCH	POSITION	LAMP.
SWITCH 1	SWITCH 2	CONDITION.
OFF	OFF	OFF
ON	OFF	ON
OFF	OFF ON	ON
ON	ON	OFF

Use : It provides flexibility and is more convenient for a person. It also encourages one to save electricity.

Conclusion : The staircase wiring was completed and tested.